

CS2100 Computer Organisation

Lab #9: Decoder

(Week 11: 30 October - 3 November 2023)

[This document is available on Canvas and course website <https://www.comp.nus.edu.sg/~cs2100>]

**Remember to
bring this along
to your lab!**

Name: _____

Student No: _____

Lab Group: _____

Important: You should complete the report before you come for your lab or you may not have enough time to complete it.


Objective:

In this experiment, you will use the decoder to implement some logic functions.

IC chips:

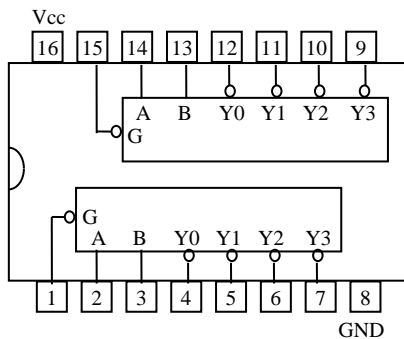1. One **74LS139** chip (DUAL 2×4 decoder with negated output and zero-enable).
2. One **74LS20** chip (DUAL 4-input NAND gates).

The decoder chip you will use in this lab is the 74LS139, which contains two sets of 2×4 decoder with *negated outputs* and *zero-enable*. The pin configuration and the function table are given below.




Function Table of 74LS139

INPUTS			OUTPUTS			
Enable	Select					
G	B	A	Y0	Y1	Y2	Y3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

1 = High, 0 = Low, X = don't care

 The 74LS20 chip contains two 4-input NAND gates. The pin configurations are shown below.



74LS20

Propagation delay:

Assume that the propagation delay for every NAND gate in 74LS20 is 15 ns (nano-seconds), and the propagation delay for each decoder in 74LS139 is 35 ns.

Procedure:

1. Given a 3-variable function $S(P,Q,R) = (P + Q + R) \cdot (P + Q') \cdot (P' + R)$, write this function in the **product-of-maxterms** form, using the ΠM notation. [1 mark]


$$S(P,Q,R) = \Pi M (\underline{\hspace{2cm}})$$

2. Complete the truth table for S below. [1 mark]

P	Q	R	S
0	0	0	0
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

 3. With the truth table above, implement function S using the 2×4 decoders in the 74LS139 chip, and NAND gates in the 74LS20 chip. Connect the inputs P , Q , and R to SW7, SW6 and SW5 on your logic trainer respectively.

Complete the following logic diagram. [5 marks]




4. Show your implementation implementation of the above circuit to your labTA before dismantling the circuit and moving on to another circuit in step 7. [5 marks]
5. What is the propagation delay of your circuit above? ns. [1 mark]

6. Given a 4-variable function $F(W,X,Y,Z) = \prod M(3, 7)$, write out the simplified SOP expression for F below. [2 marks]

Simplified SOP expression: $F =$ _____

7. Use the block diagram below to illustrate how you might implement F using only **ONE** such 2×4 decoder (with negated output and zero-enable), without any additional logic gate. Due to time constraint, you are NOT required to actually implement this circuit on the logic trainer.


Complete the diagram below. [2 marks]

 

 8. Using one 4:1 multiplexer and one 2×4 decoder with 1-enable as shown below, show how you might implement function $G(A,B,C,D) = \sum m(0, 6, 9, 15)$ without using any additional logic gate. Complete the diagram below. [3 marks]

Note that the selector lines for the 4:1 multiplexer have been fixed to AB , and you must not change it.

You do not need to implement this since you are not given any multiplexer in this lab.



Marking Scheme: Report (15 marks), Circuit (5 marks); Total: 20 marks.
Your graded report will be returned to you at the next lab.